

Total Pages – 4

B.Sc. RNLKWC-/C2T/22

2022

BCA (Hons)

B.Sc. First Semester End Examination - 2022

PAPER - C2T

Computer fundamdntal and Digital Electronics

Full Marks : 40

Time : 2 hours

*The figures in the right-hand margin indicate marks.
Candidates are required to give their answers in their own
words as far as practicable.
Illustrate the answers wherever necessary.*

Group-A

1. Answer any five questions : 5×2=10
- a) What is Digital Computer?
- b) What do you mean by application software? Give an example.

(Turn Over)

(2)

- c) What are the Software and Hardware?
- d) What is linker and loader?
- e) What is the advantage of 2's Complement?
- f) What is the limitation S-R Flip-Flop?
- g) What is bus in computer system?
- h) Convert $(12)_{10} = (?)_2$

2. Answer any four question. 5×4=20

- a) Differentiate between RAM and ROM. 5
- b) What is sequential circuit? Discuss about half subtractor.

2+3

- c) Construct circuit from the following expression using universal gate -

(3)

(i) $X.Y + \bar{X}\bar{Y}$

(ii) $\bar{A}B + (\bar{A}+B)$ 2½+2½

- d) Design the logic circuit of 8×3 Encoder with truth table.

- e) Using 7's complement, find -

$(7605)_8 - (100)_8 = (?)_8$

And write down the procedure.

- f) Design XOR and XNOR gate using NAND gate. 2½+2½

- 3. Answer any one question - 10×1=10

- a) Find the Boolean expression of

$F(A,B,C,D) = \Sigma(2,3,5,7,9,14,15)$.

Design the logic circuit and true table of J-K Flip-Flop.

What are the Master-Slave Flip-Flop? 3+5+2

(4)

b) Write short note (any two) :

5+5

(i) Big data

(ii) Cloud computing

(iii) Bluetooth

(iv) Embedded System
