

2022

Physics

[HONOURS]

(CBCS)

(B.Sc. Third Semester End Examinations-2022)

PAPER-CC7P

(PRACTICAL)

Full Marks: 20**Time: 02 Hrs**

*The figures in the right hand margin indicate marks
Candidates are required to give their answers in their own words as
far as practicable*

Illustrate the answers wherever necessary

Answer any one from the following Digital system and
Application Lab:-

1. Design a NOT gate using transistor and verify the truth table

a) Theory	5
b) Showing the result and noting the truth table	6
c) Result and discussions	4
2. Design and verify AND, OR, NOT gates using NAND gate IC's-

a) Theory	2+2+2
b) Noting the truth table and showing the result	2+2+2
c) Result and discussions	3
3. Convert the following Boolean expression into logic circuit and design it using logic gate IC's $y = \sum m(1,3,5,7)$

a) Theory	6
b) Showing the result and noting the truth table.	7
c) Result and discussions	2
4. Construct OR, AND gate using Discrete components.	
a) Theory	2
b) Circuit diagram	3+3
c) Noting the truth table and showing the result.	3
d) Result and discussions	2+2
5. Design and verify the logic identity.	
$AB + AC + BC = AC + BC$	
a) Circuit diagram.	6
b) Noting truth table and showing the result.	6
c) Result and discussions	3
6. To design Half adder circuit and to verify respective truth tables.	
a) Theory	2
b) Circuit diagram	4
c) Noting the truth table and showing the result.	6
d) Result and discussions	3
7. To design Full adder circuit and to verify respective truth tables.	
e) Theory	2
f) Circuit diagram	6
g) Noting the truth table and showing the result.	4
h) Discussions	3
8. Design a RS flip flop using NAND gates and demonstrate the excitation table.	
a) Theory	6
b) Showing the result and noting the truth table.	5
c) Result and discussions	4

9. Design a JK flip flop using NAND gates and demonstrate the excitation table.	
d) Theory	6
e) Showing the result and noting the truth table.	7
f) Result and discussions	2
10. Design and verify the truth table of a 4 bit counter using JK flip-flop (IC 7476)	
a) Theory	3
b) Circuit diagram	2+2
c) Showing the result and noting the truth table.	3+3
d) Result and discussions	2
11. Design a JKMS flip-flop using NAND gates and demonstrate the excitation table.	
a) Theory	6
b) Showing the result and noting the truth table.	5
c) Result and discussions	4
12. Design ia Astable multivibrator using IC 555.	
a) Theory	2
b) Calculation for four different set of frequencies (R_A, R_B, C)	4
c) Circuit diagram	3
d) Result	4
e) Discussions	2

I.NB - 02

VIVA - 03
