

End Semester Examination, 2022**Semester - III****Physics****PAPER - CC-7T**

Full Marks : 40

Time : 2 Hours

The Figures in the right hand margin indicate marks. Candidates are required to give their answers in their own words as far as practicable.

Group - A

1. **Answer any five questions :** **5x2=10**
- a) Represent $(2^{11}-1)$ in binary and hexa-decimal. 2
- b) Subtract by 2's compliment method
- i) 1101 from 1110
- ii) 1001 from 1101. 1+1=2
- c) What do you know by duty cycle of a clock? 2
- d) Proof the following using Boolean algebraic theorems.
- $$\overline{AB} + \overline{A} + AB = 1 \quad 2$$
- e) What is RAM and ROM? 2
- f) What is the function of time-base circuit in CRO?
- g) What is race around condition in JK flip-flop?
- h) How phase difference between two voltages can be measured using CRO?

(Turn Over)

Group - B**Answer any four questions : 4x5=20**

2. a) What is multiplexer? Draw a logic block diagram of a 4:1 multiplexer. 1+1
 b) Explain the operation of basic sequential circuit (S-R latch) 3
3. a) Give difference between racing and toggling. 2
 b) Write down the Boolean function corresponding to the following standard POS notation : 3
 $f(A, B, C) = \Pi M(0, 1, 2, 5)$
4. a) Explain performance of a 4-bit subtractor using 4 bit adder (use full adder) 3
 b) Show how to implement an AND gate with OR and NOT gates. 2
5. a) Classify counters. How many flip flops do you need to count numbers (0-31) 1+1
 b) Convert D3B to its octal equivalent. 1
 c) Distinguish between ripple counter and synchronous counter. 2
6. Design an astable multivibrator using 555 timer for a frequency of 1 KHz and a duty cycle of 70%. 5
7. a) What is the deflection sensitivity in CRO?
 b) The period of the time-base of CRO is 1ms.
 Find the number of waveforms obtained on the screen if the frequency of the vertical input voltage is 1KHz. 2+3

Group - C**Answer any one questions : 1x10=10**

8. a) What is a Karnaugh map? What you mean by don't care cells? 1+1
 b) Simplify the Boolean function 4
 $f(W, X, Y, Z) = \sum m(1, 2, 4, 7, 13) + d(9, 11, 14)$
 c) Draw a negative edge triggered J-K flip flop system using universal gate. Explain its operation. 1+3
9. a) Draw a logic diagram of a BCD-encoder and explain its operation. 5
 b) Obtain the Boolean expression for the output Y in the logic circuit of that figure. Simplify the expression and show that the circuit is equivalent to an AND gate with inputs A and B. 5

