

2021
BCA
[HONOURS]
(CBCS)
(B.Sc. First Semester End Examination-2021)
PAPER-C2T

Full Marks: 40

Time: 02 Hrs

The figures in the right hand margin indicate marks
Candidates are required to give their answers in their own words as
far as practicable
Illustrate the answers wherever necessary

- 1. Answer any five questions of the following: 5x2= 10**
- Write down the difference between SRAM and DRAM.
 - Solve the following:
 - $(1011)_2 + (10111)_2 = (?)_2$
 - $(247)_8 + (142)_8 = (?)_8$
 - convert $(201.21)_8 = (?)_{10}$
 - What is Bubbled AND gate?
 - Simplify the following Expression-
 $(AB + ABC) \square \bar{A}\bar{B}C$
 - What is primary memory?
 - What is the function of multiplexer?

h. Write the name of various type of Flip-flop.

2. Answer any four questions of the following: 5x4 = 20

a) Write down the comparison between Assembler, compiler and interpreter.

b) Write a short note on CPU of a computer.

c) What is combinational logic circuit? Discuss about half adder.
1+4

d) Construct the following gates from universal NOR gate:

i) XOR

ii) AND

Also write the truth table for each.

e) Find the K-map of XOR and XNOR gate. What is half adder ?
2.5+2.5

f) Draw the circuit diagram of decoder (3x8) and find it's Boolean expression.

g) Find 1's and 2's complement of $(-45)_{10}$. Compare between 1's and 2's complement.

h) Short note: J-K flip flop and T flip flop

3. Answer any one questions of the following: 10x1 = 10

a) Build an expression and simplify the following function –

$$f(A, B, C) = \prod(0, 4, 5, 6)$$

Also, draw a circuit diagram (using basic gate) of the simplified expression. 5+5

b) Write short note of the following (any four)

i) Universal gates

ii) Encoder

iii) Shift Register

iv) Ripple Counter

v) De-multiplexer 2.5x4
